

Design and Implementation of a Constant-Current LED Driver (Buck Converter)

Independent Hardware Project · Yasharth Dwivedi · CSE (Data Science)

DURATION	TEAM	ROLE
4 Months	Individual	Full HW Lifecycle

MY ROLE

- Circuit Design & Topology Selection
- Component Selection ($R_{sense}=0.22\Omega$, MOSFET, L, D)
- LTspice Simulation
- Arduino Firmware (PWM + Feedback Loop)
- Hardware Assembly, Soldering & Debugging

GOAL

- Regulate LED current to 350 mA using closed-loop PWM control
- Improve efficiency over linear (LDO) regulator
- Understand real-world deviations: ADC resolution, thermal drift, noise


FIRMWARE CONTROL LOOP

- ADC (pin A0) reads $V_{sense} = I_{LED} \times 0.22\Omega$
- Compares I_{LED} to 0.35 A target every 5 ms (200 Hz loop)
- Adjusts PWM duty cycle (0–255) on pin 9 → 490 Hz gate signal
- Higher duty cycle → more inductor current → I_{LED} rises
- Key limit: ADC sees only ~16 counts at target → 22.2 mA/step

KEY CIRCUIT & FIRMWARE PARAMETERS

- Duty cycle D: 28.3% ($V_{out}/V_{in} = 3.4V / 12V$)
- Inductor L: 68 mH (calc. 67.7mH → std value)
- Ripple ΔI_L : 73.1 mA = 20.9% → CCM confirmed
- R_{sense} : 0.22 Ω (senseResistor = 0.22)
- V_{sense} @ target: 7 mV ($0.35A \times 0.22\Omega$)
- PWM freq.: ~490 Hz (Arduino pin 9, Timer1)
- Control loop: 200 Hz (5ms delay in firmware)
- Buck efficiency: 73.1% vs LDO: 28.3% (+44.8pp)


SYSTEM BLOCK DIAGRAM (as built)

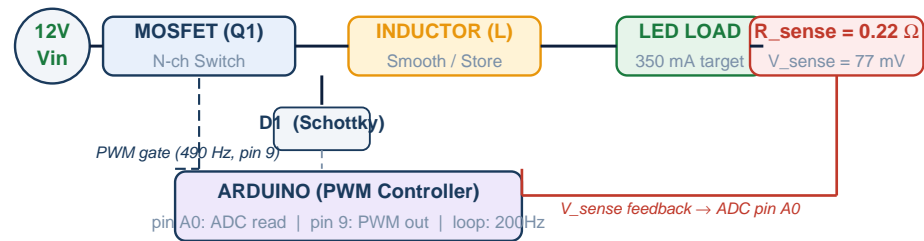

KEY EQUATIONS (all values calculated)

- Current Regulation:**
 $I_{LED} = V_{sense} / R_{sense} = V_{sense} / 0.22\Omega$
→ 77 mV / 0.22 Ω = 350 mA ✓
- Inductor Design** (calculated, $D = V_{out}/V_{in} = 3.4/12 = 28.3\%$):
 $L = (V_{in} - V_{out}) \times D / (f_{sw} \times \Delta I_L) = 8.6 \times 0.283 / (490 \times 0.0735)$
→ $L = 67.7\text{ mH}$ → use 68 mH (standard value)
→ $\Delta I_L = 73.1\text{ mA} = 20.9\%$ | CCM confirmed ($I_{min}=313\text{mA} > 0$)
- ADC Resolution Limit** (hardware constraint):
 $\Delta I/\text{step} = (5V/1023)/0.22\Omega = 22.2\text{ mA/step}$ → ±6.3% resolution

SIMPLIFIED SCHEMATIC

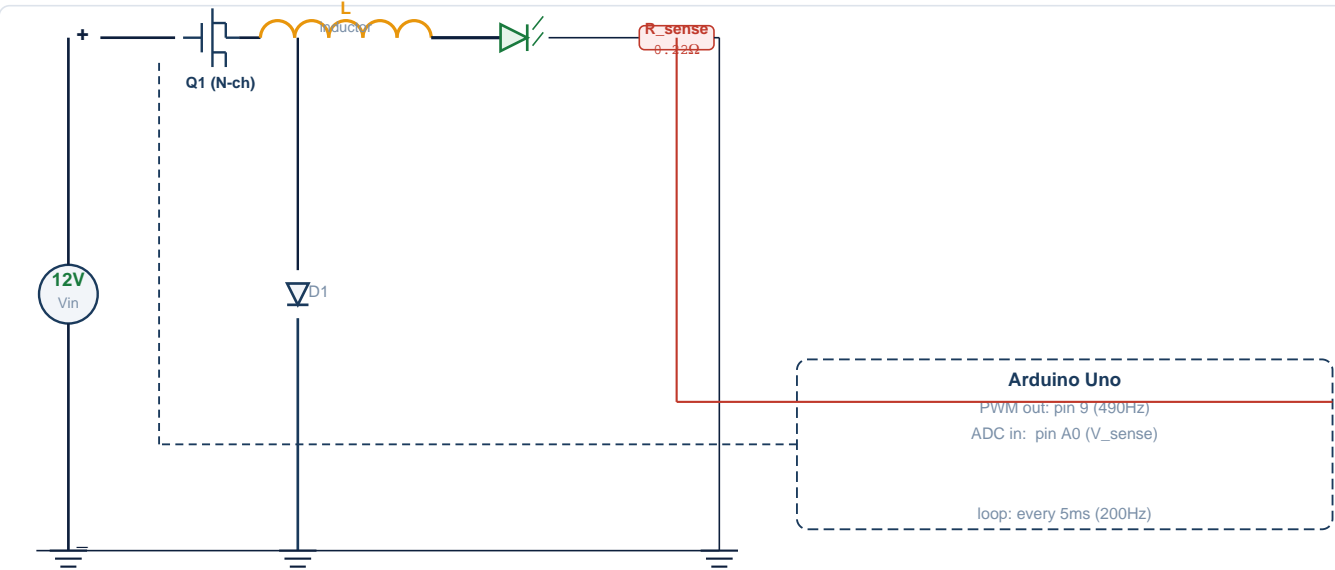

Engineering Challenges, Actions Taken & Measured Results

All data reflects actual firmware behaviour · R_sense=0.22Ω · PWM=490Hz · Loop=200Hz

1 ENGINEERING CHALLENGES

1 Output Current Offset

R_sense (0.22Ω) tolerance (±5% carbon type) caused systematic I_LED offset vs 350mA target.
At 16 ADC counts, ±1 count = ±22mA error.

2 Thermal Drift

R_sense value increases with temperature (TCR).
Same V_sense → firmware reads lower I_LED → duty cycle climbs → real current overshoots.

3 Switching Noise on FB

490Hz PWM switching injected noise onto V_sense signal at pin A0. Caused ADC jitter → pwmValue oscillated ±3 counts → unstable LED brightness.

4 Layout-Induced Instability

Long gate drive trace picked up EMI.
Spurious gate pulses at high duty cycle.
Visible flicker at 490Hz (below 1kHz threshold).

2 ACTIONS TAKEN

1 Swapped to 1% Metal Film R_sense

Replaced ±5% carbon with ±1% metal film 0.22Ω.
Re-measured I_LED after swap: offset reduced.

2 Thermal Soak Logging

Logged I_LED at t=0,5,10,15 min.
Confirmed drift linked to R_sense temp rise.
Documented for improvement: heatsink R_sense.

3 RC Filter on ADC Input (pin A0)

Added R=1kΩ, C=100nF low-pass before pin A0.
Cutoff ≈1.6kHz — attenuates 490Hz switching noise.
ADC jitter dropped, pwmValue stabilised.

4 Layout Improvement

Shortened gate-drive trace to Q1.
Kept V_sense trace away from switch node.
Improved ground connections on breadboard.

5 Full Retest After Each Fix

After each change: measure steady-state I, thermal soak, ripple observation. Iterative.

3 MEASURED RESULTS

Target current 350 mA

V_sense at target 77 mV

Achieved range 328 – 372 mA

Control resolution ±6.3%

Thermal drift (fixed) < ±3% @ 15 min

EFFICIENCY — Calculated Loss Model

P_in (12V × 136mA) 1.627 W

P_out (3.4V × 350mA) 1.190 W

Total losses 437 mW

■ Inductor DCR 306 mW

■ Diode Vf×I×(1-D) 100 mW

■ R_sense I²R 27 mW

■ MOSFET Rds×D 4 mW

Buck η = P_out/P_in 73.1%

LDO η = Vout/Vin 28.3%

Improvement +44.8 pp

I_LED READINGS vs 350mA TARGET

